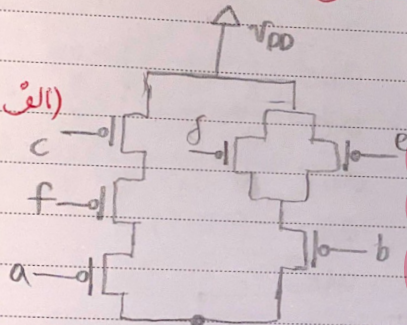


۹۹۴۶۲۴۱۴۶ سکه سر


الف



-5 for do not draw "a"
Transistor in a correct place

+15

۲

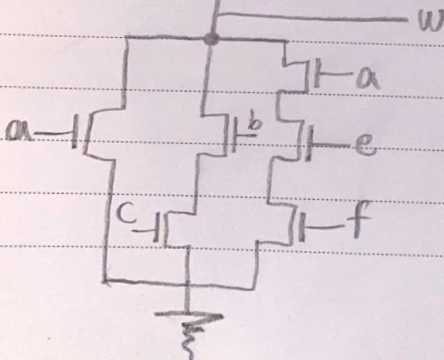

ب) $f = a + (b + (ed))(c + f)$

+7

-8 for did not put NOT
in the function

TANDIS