
ابوالعقيل شارك. سوال ادل-

J=a.b.c+d

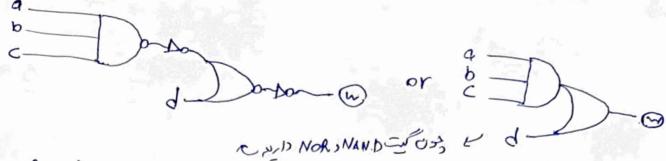

Complengate:

-15 for not implement complex and optimize approach

