
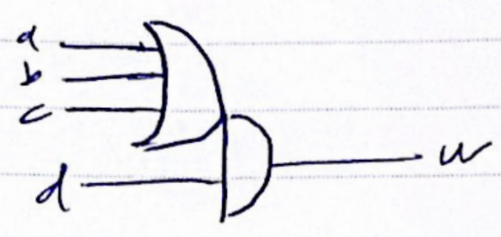


Subject: _____
Year: _____ Month: _____ Date: _____

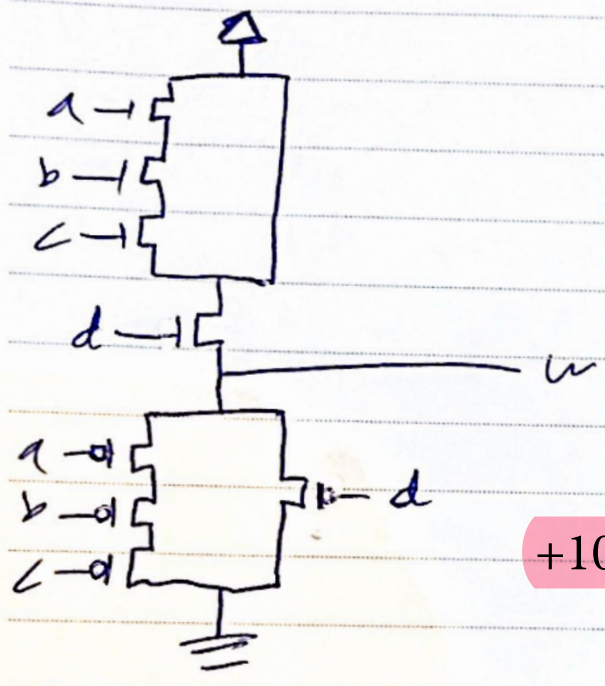$F = (a + b + c) d$
nmos # (۴, ۴, ۵)
pmos # (۵, ۶, ۷)



الف



-5 for didn't put NOT in inputs
-5 for use extra NOT gates

+10